

Introduction to VHDL

Dr. Adnan Shaout

The University of Michigan-Dearborn

Objective

- Quick introduction to VHDL
 - basic language concepts
 - basic design methodology
 - examples

VHDL

Very Hard Difficult Language

jk -- VHDL

VHSIC Hardware
Description Language

VHSIC --
Very High Speed Integrated Circuits

Modeling Digital Systems

- VHDL is for coding models of a digital system...
- Reasons for modeling
 - requirements specification
 - documentation
 - testing using simulation
 - formal verification
 - synthesis
 - class assignments
- Goal
 - most ‘reliable’ design process, with minimum cost and time
 - avoid design errors!

Basic VHDL Concepts

- Interfaces -- i.e. ports
- Behavior
- Structure
- Test Benches
- Analysis, simulation
- Synthesis

VHDL --

- VHDL is a programming language that allows one to model and develop complex digital systems in a dynamic environment.
- Object Oriented methodology for you C people can be observed -- modules can be used and reused.
- Allows you to designate in/out ports (bits) and specify behavior or response of the system.

VHDL Intro.--

- Oh yeah, For all you C people --forget everything you know...
- Well, not EVERYTHING ...
- But VHDL is NOT C ...
There are some similarities, as with any programming language, but syntax and logic are quite different; so get over it !!

-obviously, this was a painful transition for me.

3 ways to DO IT -- the VHDL way

- Dataflow
- Behavioral
- Structural

Kindof BORING sounding huh??

well, it gets more exciting with the details !!

:)

Modeling the Dataflow way

- uses statements that defines the actual flow of data.....

such as,

```
x <= y      -- this is NOT less than equal to  
            -- told you its not C
```

this assigns the boolean signal x to the value of
boolean signal y... i.e. $x = y$
this will occur whenever y changes....

Jumping right in to a Model -- e.g. 1

- lets look at a d - flip-flop model -- doing it the dataflow way.....
ignore the extra junk for now --

entity dff_flow **is**

```
port (      d      :in  bit;
        prn      :in  bit;
        clrn     :in  bit;
        q        :out bit;
        qbar     :out bit;
    );
```

end dff_flow;

architecture arch1 **of** dff_flow **is**

begin

```
q <= not prn Or (clrn And d);    % this is the DATAFLOW %
qbar <= prn And (not clrn Or not d);  % STUFF  %
```

end arch1;

-----Dr. Adnan Shaout

library ieee; use ieee.std_logic_1164.all;

entity fulladd is

port(A1,A2,Cin: IN std_logic;

Sum, Cout: OUT std_logic);

end fulladd;

Architecture a of fulladd is

Begin

process(A1,A2,Cin)

Begin

Sum <= Cin XOR A1 XOR A2;


Cout <= (A1 AND A2) OR (Cin AND (A1 XOR A2));

end process;

end a;

Modeling Interfaces

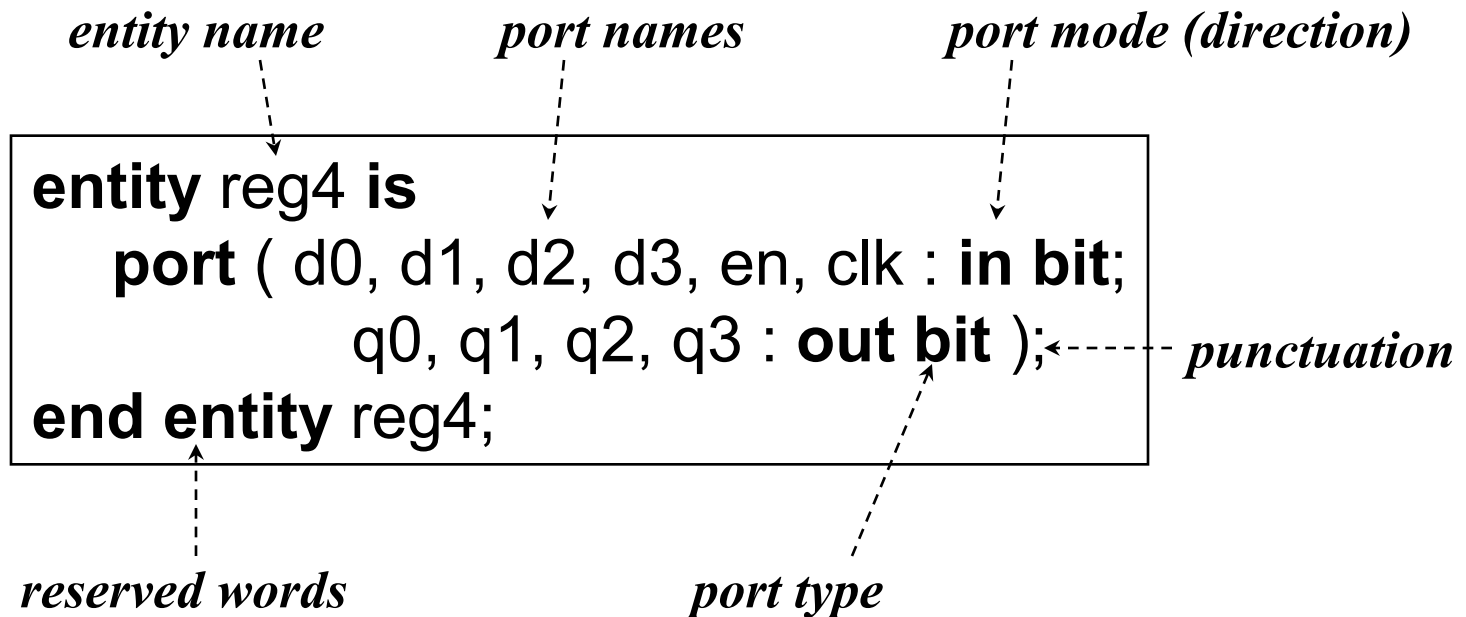- *Entity* declaration
 - describes the input/output *ports* of a module



Modeling the Behavior way

- *Architecture body*
 - describes an implementation of an entity
 - may be several per entity
- *Behavioral architecture*
 - describes the algorithm performed by the module
 - contains
 - *process statements*, each containing
 - *sequential statements*, including
 - *signal assignment statements* and
 - *wait statements*

The Behavior way -- eg 2

architecture behav **of** reg4 **is**

begin

process (d0, d1, d2, d3, en, clk) *sensitivity list*
 variable stored_d0, stored_d1, stored_d2, stored_d3 : bit;

begin

if en = '1' **and** clk = '1' **then**

 stored_d0 := d0;

 stored_d1 := d1;

 stored_d2 := d2;

 stored_d3 := d3;

*notice := syntax
used for equating values
from signals...*

end if;

 q0 <= stored_d0 **after** 5 ns;

 q1 <= stored_d1 **after** 5 ns;

 q2 <= stored_d2 **after** 5 ns;

 q3 <= stored_d3 **after** 5 ns;

*simulates real-world
propagation delays.*

end process;

end behav;

VHDL -- goofy syntax to know..

- Omit **entity** at end of entity declaration
- Omit **architecture** at end of architecture body
- Omit **is** in process statement header


```
entity reg4 is  
port ( d0, d1, d2 : in bit  
        d3, en, clk : in bit;  
        q0, q1, q2, q3 : out bit  
        );  
end reg4;
```

```
architecture behav of reg4 is  
begin  
    process (d0, ... )  
        ...  
    begin  
        ...  
    end process ;  
end behav;
```


Modeling the Structural way

- *Structural* architecture
 - implements the module as a composition of subsystems
 - contains
 - *signal declarations*, for internal interconnections
 - the entity ports are also treated as signals
 - *component instances*
 - instances of previously declared entity/architecture pairs
 - *port maps* in component instances
 - connect signals to component ports

Structural way -- e.g. 3

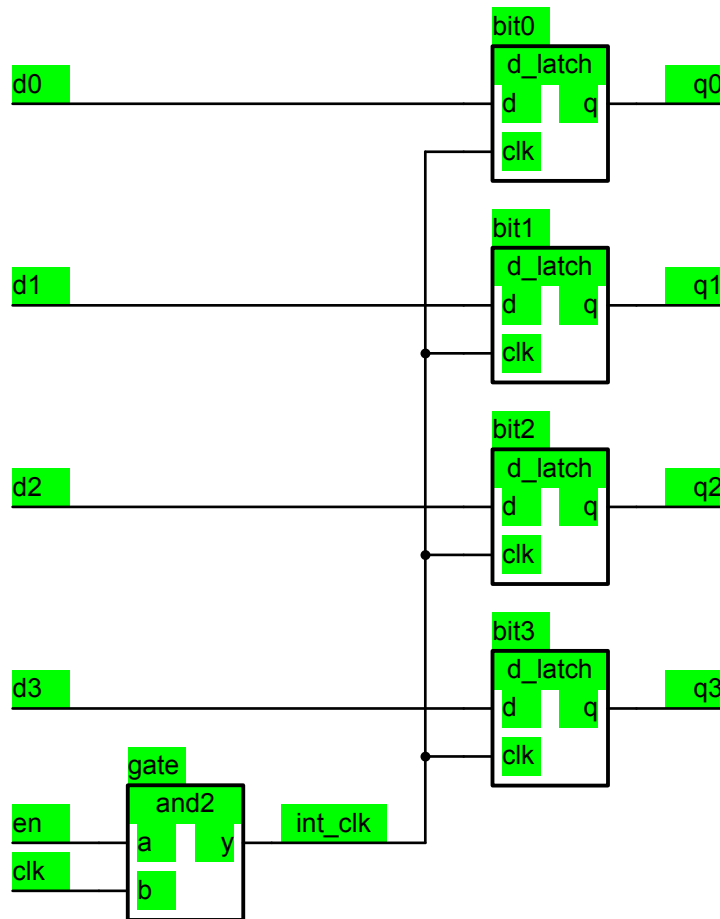

Structural way cont..

- First declare D-latch and and-gate entities and architectures

notice semicolon placements -- odd as it is, omit from last statement

```
entity d_latch is  
    port ( d, clk : in bit; q : out bit );  
end entity d_latch;
```

```
architecture basic of d_latch is  
begin
```

```
    process (clk, d)  
    begin  
        if clk = '1' then  
            q <= d after 2 ns;  
        end if;  
    end process;
```

```
end basic;
```

```
entity and2 is  
    port ( a, b : in bit; y : out bit );  
end entity and2;
```

```
architecture basic of and2 is  
begin
```

```
    process (a, b)  
    begin  
        y <= a and b after 2 ns;  
    end process ;  
end basic;
```

Structural way...

- Declare corresponding components in register architecture body

```
architecture struct of reg4 is  
    component d_latch  
        port ( d, clk : in bit; q : out bit );  
    end component;  
    component and2  
        port ( a, b : in bit; y : out bit );  
    end component;  
    signal int_clk : bit;  
  
    ...
```

Structural way..


- Now use them to implement the register

```
...  
begin  
    bit0 : d_latch  
        port map ( d0, int_clk, q0 );  
    bit1 : d_latch  
        port map ( d1, int_clk, q1 );  
    bit2 : d_latch  
        port map ( d2, int_clk, q2 );  
    bit3 : d_latch  
        port map ( d3, int_clk, q3 );  
    gate : and2  
        port map ( en, clk, int_clk );  
end struct;
```

Mixed Behavior and Structure

- An architecture can contain both behavioral and structural parts
 - process statements and component instances
 - collectively called *concurrent statements*
 - processes can read and assign to signals
- Example: register-transfer-level (RTL) Model
 - data path described structurally
 - control section described behaviorally

Mixed Example

 

Mixed Example

```
entity multiplier is
    port ( clk, reset : in bit;
           multiplicand, multiplier : in integer;
           product : out integer );
end multiplier;

architecture mixed of mulitplier is
    signal partial_product, full_product : integer;
    signal arith_control, result_en, mult_bit, mult_load : bit;
begin
    arith_unit : entity work.shift_adder(behavior)
        port map ( addend => multiplicand, augend => full_product,
                  sum => partial_product,
                  add_control => arith_control );
    result : entity work.reg(behavior)
        port map ( d => partial_product, q => full_product,
                  en => result_en, reset => reset );
    ...
```


Mixed Example

```
...
multiplier_sr : entity work.shift_reg(behavior)
  port map ( d => multiplier, q => mult_bit,
            load => mult_load, clk => clk );
product <= full_product;

process (clk, reset)
  -- variable declarations for control_section
  -- ...
begin
  -- sequential statements to assign values to control signals
  -- ...
end process;
end mixed;
```

Test Bench your Model

- Testing a design by simulation
- Use a *test bench* model
 - a Model that uses your Model
 - apply test sequences to your inputs
 - monitors values on output signals
 - either using simulator
 - or with a process that verifies correct operation
 - or logic analyzer

Analysis

- Check for syntax and logic errors
 - syntax: grammar of the language
 - logic: how your Model responds to stimuli
- Analyze each *design unit* separately
 - entity declaration
 - architecture body
 - ...
 - put each design unit in a separate file -- *helps a lot.*
- Analyzed design units are placed in a *library*
 - make sure your Model is truly OOP

Simulation

- Discrete event simulation
 - time advances in discrete steps
 - when signal values change—*events* occur
- A processes is *sensitive* to events on input signals
 - specified in wait statements
 - resumes and schedules new values on output signals
 - schedules *transactions*
 - *event* on a signal if value changes


Simulation Algorithm

- Initialization phase
 - each signal is given its initial value
 - simulation time set to 0
 - for each process
 - activate
 - execute until a wait statement, then suspend
 - execution usually involves scheduling transactions on signals for later times

Simulation Algorithm

- Simulation cycle
 - advance simulation time to time of next transaction
 - for each transaction at this time
 - update signal value
 - event if new value is different from old value
 - for each process sensitive to any of these events, or whose “wait for ...” time-out has expired
 - resume
 - execute until a wait statement, then suspend
- Simulation finishes when there are no further scheduled transactions

Basic Design Methodology

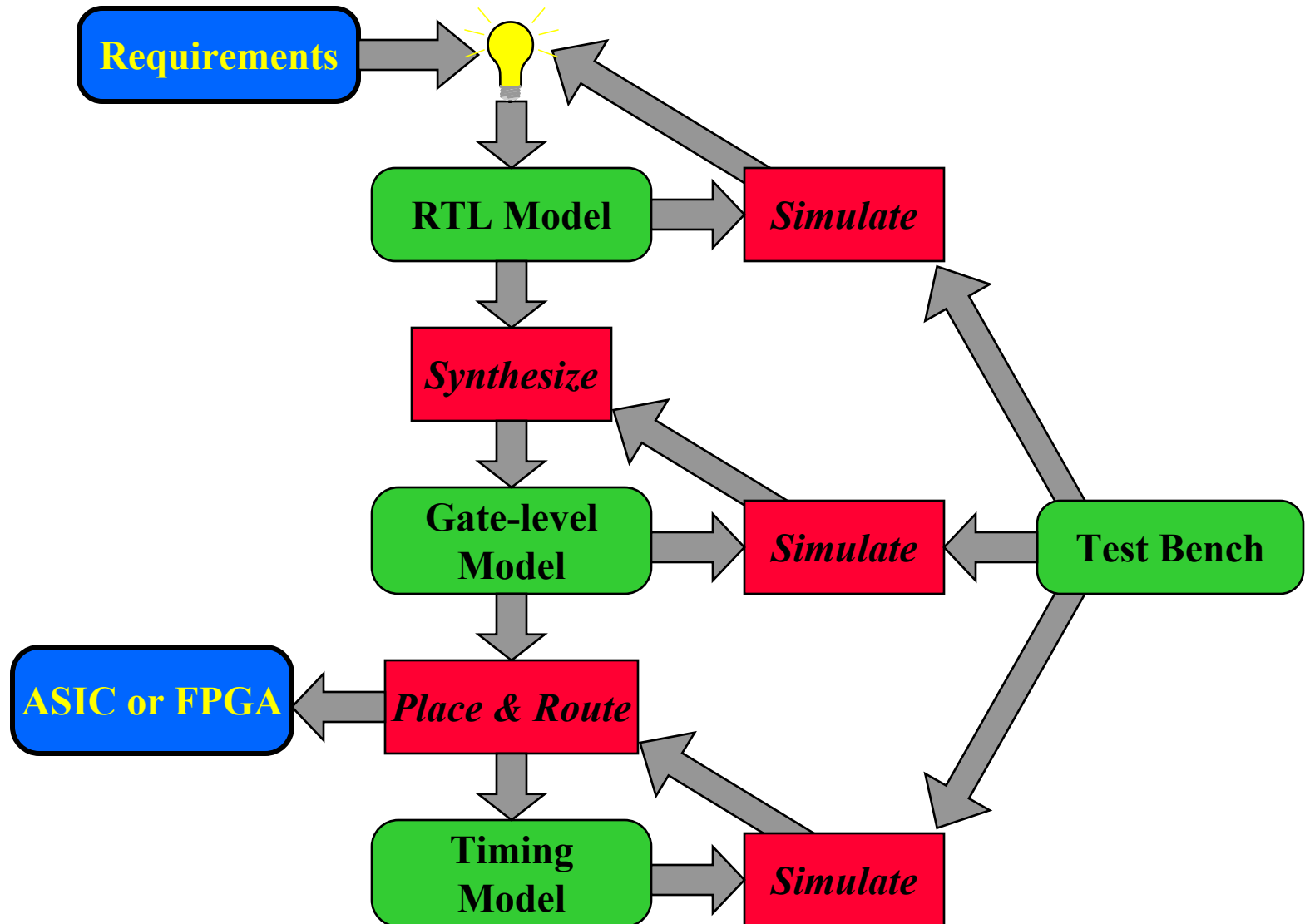

VHDL -- conclusion...

- Thats it !! in review -- replay presentaion
- Now for first asignment design a computer
 - Memory access
 - processor
 - data/address bus
 - display
- Always remember to use this knowledge for GOOD...